

CSE4356/CSE5392/EE4328/EE5315 System on Chip Fall 2025, Lab 1

This lab is due by September 18, 2025. In this lab, you will write Verilog code and configure the Blackboard to implement a 4-nibble hexadecimal counter.

The following steps will guide you through this process:

1. Create a module, `hex_to_ss`, that converts a 4-bit hexadecimal number to a 8-bit output that is compatible with the format required to driver the cathodes of the seven segment display.
2. Create a module, `seven_seg`, that accepts a clock input, multidimensional display data (8-bits for each of the 4 seven-segment displays), a 4-bit output to drive the anodes, and an 8-bit output to drive the cathodes. The module should repeatedly cycle through the 4 seven-segment displays driving one anode at a time while time multiplexing the correct display data to the cathodes. The module should cycle through the 4 anodes fast enough to avoid any flicker.
3. Instantiate the module from (2) and instantiate 4 `hex_to_ss` modules from (1) to drive the display data of the `seven_seg` module.
4. Add a 16-bit counter that drives the 4 `hex_to_ss` modules so that the modules output the display data to drive the 4 seven segment displays with the `seven_seg` module. The counter should initially increment by one every 250ms.
5. Safely condition the `PB[0]` input and add logic to reset the counter when `PB[0]` is pressed.
6. Safely condition the `SW[11]` input and add logic so the counter increments if `SW[11]` is '1' and decrements if `SW[11]` is '0' every 250ms.
7. Safely condition `SW[10:0]` to form a value `DELTA`. Change the counter to increment or decrement by `DELTA` every 250 ms.
8. Safely condition the `PB[1]` and `PB[2]` inputs. Add logic so that a value `MINIMUM` is set to the current counter value when `PB[1]` is pressed. Add logic so that a value `MAXIMUM` is set to the current counter value when `PB[2]` is pressed. Add logic so that the default `MINIMUM` and `MAXIMUM` are 0x0000 and 0xFFFF on reset. The counter should only count in the range `[MINIMUM, MAXIMUM]`. Make sure to handle all `DELTA` values correctly, including a zero value. How to handle the wrap around values when `DELTA` is not an integer sub-multiple of `MAXIMUM-MINIMUM+1` is left for implementer.
9. Safely condition the `PB[3]` input. Add logic so that a value `MATCH` is set to the current counter value when `PB[3]` is pressed.
10. Add logic so that `LED[0]` toggles when the counter value is equal to `MATCH`.